

Εργαστηριακή Άσκηση 5

ΧΡΗΣΤΟΣ ΚΟΥΤΟΥΛΗΣ ΑΜ:5064

ΜΑΡΙΑ ΚΑΤΩΛΗ, ΑΜ:5083

ΟΜΑΔΑ 18


Μέρος 1^ο: Συνδυαστικά κυκλώματα

Ερώτημα 1^ο

Ο κώδικας για τον πολυπλέκτη 4 σε 1:

```
1 library IEEE;
2 use IEEE.std_logic_1164.all;
3 entity MUX4_1 is
4 port ( D : in std_logic_vector (3 downto 0);
5       SEL: in std_logic_vector (1 downto 0);
6       Y: out std_logic);
7 end MUX4_1;
8 architecture RTL4_1 of MUX4_1 is
9 begin
10 Y <= D(0) when SEL="00" else D(1) when SEL="01" else D(2) when SEL="10" else D(3);
11 end RTL4_1;
```

Η εξομοίωση:

 


Ερώτημα 2^ο:

Ο κώδικας για τον πολυπλέκτη 16 σε 1:

```
1 library IEEE;
2 use IEEE.std_logic_1164.all;
3
4 entity MUX16_1 is
5 port ( D : in std_logic_vector (15 downto 0);
6       SEL: in std_logic_vector (3 downto 0);
7       Y: out std_logic);
8 end MUX16_1;
9
10 architecture RTL of MUX16_1 is
11 component MUX4_1
12 port ( D : in std_logic_vector (3 downto 0);
13       SEL: in std_logic_vector (1 downto 0);
14       Y: out std_logic );
15 end component;
16 signal F : std_logic_vector (3 downto 0);
17 begin
18 u0: MUX4_1 port map (D => D(3 downto 0), SEL => SEL(1 downto 0), Y => F(0));
19 u1: MUX4_1 port map (D => D(7 downto 4), SEL => SEL(1 downto 0), Y => F(1));
20 u2: MUX4_1 port map (D => D(11 downto 8), SEL => SEL(1 downto 0), Y => F(2));
21 u3: MUX4_1 port map (D => D(15 downto 12), SEL => SEL(1 downto 0), Y => F(3));
22 u4: MUX4_1 port map (D => F(3 downto 0), SEL => SEL(3 downto 2), Y => Y);
23 end RTL;
```

Η εξομίωση:

 

Η μέγιστη καθυστέρηση είναι 12.247ns:

Propagation Delay						
	Input Port	Output Port	RR	RF	FR	FF
1	D[0]	Y	11.859	11.859	11.859	11.859
2	D[1]	Y	11.451			11.451
3	D[2]	Y	11.673	11.673	11.673	11.673
4	D[3]	Y	11.170			11.170
5	D[4]	Y	11.852	11.852	11.852	11.852
6	D[5]	Y	12.155	12.155	12.155	12.155
7	D[6]	Y	8.937			8.937
8	D[7]	Y	11.743			11.743
9	D[8]	Y	11.621	11.621	11.621	11.621
10	D[9]	Y	11.452			11.452
11	D[10]	Y	11.756			11.756
12	D[11]	Y	11.090			11.090
13	D[12]	Y	11.636	11.636	11.636	11.636
14	D[13]	Y	11.813			11.813
15	D[14]	Y	11.957			11.957
16	D[15]	Y	11.809			11.809
17	SEL[0]	Y	12.247	12.247	12.247	12.247
18	SEL[1]	Y	9.476	9.476	9.476	9.476
19	SEL[2]	Y	11.246	11.246	11.246	11.246
20	SEL[3]	Y	11.221	11.707	11.707	11.221

Ερώτημα 3º:

Ο κώδικας για τον πλήρη αθροιστή:

```
1 library IEEE;
2 use IEEE.std_logic_1164.all;
3 entity FULLADDER is
4 port (A,B,Cin : in std_logic;
5       Y, Cout: out std_logic);
6 end FULLADDER;
7
8 architecture behaviour of FULLADDER is
9 begin
10 Y<= (A XOR B) XOR Cin;
11 Cout<= (A XOR B) AND Cin OR (A AND B);
12 end behaviour;
13
```

Ο κώδικας για τον αθροιστή 8 δυαδικών ψηφίων:

```
1  library IEEE;
2  use IEEE.std_logic_1164.all;
3  entity Adder8 is
4  port ( A, B : in std_logic_vector (7 downto 0);
5        Cin : in std_logic;
6        Y: out std_logic_vector (7 downto 0);
7        Cout: out std_logic );
8
9  end Adder8;
10 architecture RTL of Adder8 is
11 component FULLADDER
12 port (A,B,Cin : in std_logic;
13       Y, Cout: out std_logic);
14 end component;
15 signal F: std_logic_vector (6 downto 0);
16 begin
17   u0: FULLADDER port map(A(0),B(0),Cin,Y(0),F(0));
18   u1: FULLADDER port map(A(1),B(1),F(0),Y(1),F(1));
19   u2: FULLADDER port map(A(2),B(2),F(1),Y(2),F(2));
20   u3: FULLADDER port map(A(3),B(3),F(2),Y(3),F(3));
21   u4: FULLADDER port map(A(4),B(4),F(3),Y(4),F(4));
22   u5: FULLADDER port map(A(5),B(5),F(4),Y(5),F(5));
23   u6: FULLADDER port map(A(6),B(6),F(5),Y(6),F(6));
24   u7: FULLADDER port map(A(7),B(7),F(6),Y(7),Cout);
25 end RTL;
```

Μέρος 2º:

Ερώτημα 1º:


Ο κώδικας για το D Flip Flop:

```
1  library IEEE;
2  use IEEE.std_logic_1164.all;
3  entity DFLIPFLOP is
4  port ( CLK, D, CLR, SET, EN: in std_logic;
5        Q, Qn : out std_logic );
6  end DFLIPFLOP;
7
8  architecture RTL of DFLIPFLOP is
9  signal DFF : std_logic;
10 begin
11 seq0 : process (CLK, CLR, SET, EN )
12 begin
13   if (EN='0') then DFF<='0';
14   elsif (CLR='1') then DFF<='0';
15   elsif (SET='1') then DFF<='1';
16   elsif (CLK'event and CLK = '1') then DFF <=D;
17   end if;
18 end process;
19 Q <= DFF; Qn <= not DFF;
20 end RTL;
```


Ο κώδικας για το latch:

```
1  library IEEE;
2  use IEEE.std_logic_1164.all;
3  entity MyLatch is
4  port ( Rst, Set, LE, D : in std_logic;
5        Q, Qn: out std_logic );
6  end MyLatch;
7
8  architecture RTL of MyLatch is
9  signal FF: std_logic;
10 begin
11  seq0 : process (Rst, Set, D, LE)
12  begin
13      if Rst = '1' then FF <= '0';
14      elsif Set = '1' then FF <= '1';
15      elsif LE = '1' then FF <= D;
16      end if;
17  end process;
18  Q <= FF;
19  Qn <= not FF;
20 end RTL;
```

Το σχηματικό:

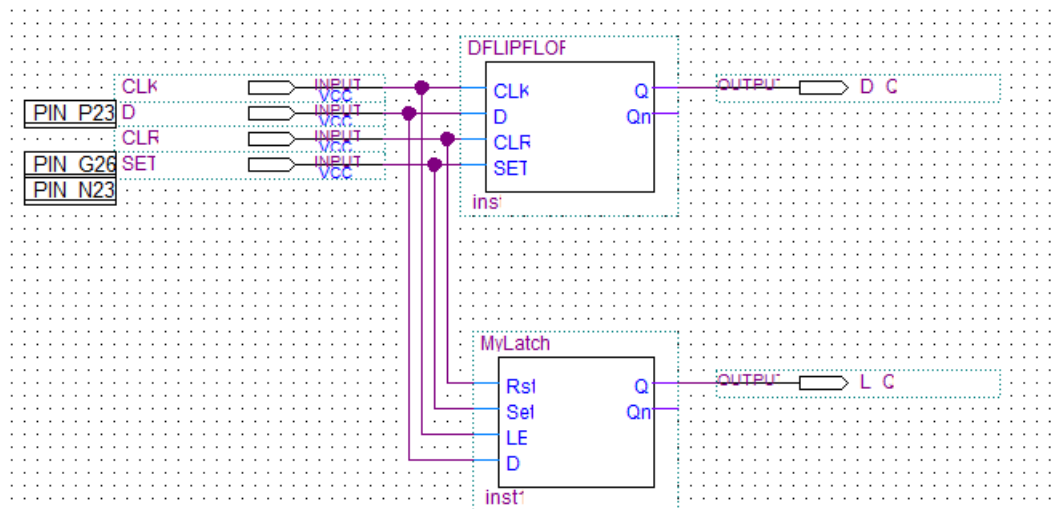

Η εξομείωση:

 


Ερώτημα 2°:

Ο κώδικας:

```
1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity Reg8 is
5  port (CLK , CLR, SET, EN: in std_logic;
6        I: in std_logic_vector(7 downto 0);
7        Q: out std_logic_vector(7 downto 0));
8  end Reg8;
9
10
11 architecture RTL of Reg8 is
12     signal DFF: std_logic_vector(7 downto 0);
13     begin
14         seq0 : process (CLK, CLR, SET)
15         begin
16             if (CLR='1') then DFF<=(7 downto 0 => '0');
17             elsif (SET='1') then DFF<=(7 downto 0 => '1');
18             elsif (CLK'event and CLK = '1' and EN='1') then DFF<=I;
19             end if;
20         end process;
21         Q <= DFF;
22     end RTL;
```

Η εξομοίωση:

 

Ερώτημα 3°:

Ο κώδικας:

```
1  library IEEE;
2  use IEEE.std_logic_1164.all;
3  use IEEE.std_logic_unsigned.all;
4
5  entity Counter8 is
6  port (CLK , CLR, SET, EN: in std_logic;
7        Q: out std_logic_vector(7 downto 0));
8  end Counter8;
9
10
11 architecture RTL of Counter8 is
12     signal sum: std_logic_vector(7 downto 0);
13 begin
14     seq0 : process (CLK, CLR, SET)
15     begin
16         if (CLR='1') then sum<=(7 downto 0 => '0');
17         elsif (SET='1') then sum<=(7 downto 0 => '1');
18         elsif (CLK'event and CLK='1' and EN='1') then sum<=(sum + '1');
19         end if;
20     end process;
21     Q<=sum;
22 end RTL;
```

Η εξομείωση:

